ASSEMBLY ASSIGNMENT

${\bf Pavan~Srinivas~Marri} \\ {\bf marripavan 65@gmail.com} \\ {\bf FWC 22138~IITH~-~Future~Wireless~Communications} \\$


Contents

1	Problem	1
2	Components	1
3	Implementation3.1 Boolean Expression3.2 Truth Table	2 2 2
4	Hardware	2
5	Software	2
6	Conclusion	3

1 Problem

(GATE2019-QP-EE)

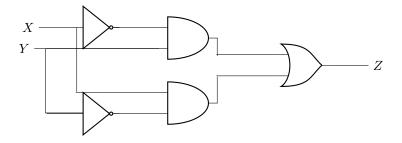Q.36 In the circuit shown below , X and Y are digital inputs, and Z is a digital output. The equivalent circuit is a



- (A) NAND gate
- (B) NOR gate
- (C) XOR gate
- (D) XNOR gate

2 Components

Components	Value	Quantity
Arduino	Uno	1
BreadBoard		1
Jumper Wires		4

Table 1: Components

3 Implementation

3.1 Boolean Expression

By solving above expression we get :

$$z = x'.y + x.y'$$
$$z = x'y + xy'$$

3.2 Truth Table

A	В	OUT
0	0	0
0	1	1
1	0	1
1	1	0

Table 2: Truth Table

4 Hardware

1. Make the connections between the arduino and Breadboard as shown in Table 3.

Arduino	5.0v	GND
Breadboard	+ve	-ve

Table 3: Connections

- 2. Connect one end of a jumper wire to the GND(ground) pin on the Arduino Uno board and other end to the breadboard's ground rail(-).
- 3. Connect one terminal of jumper wire (Input A) to the input pins on the Arduino(e.g., pin2) and other terminal to the positive rail(+) on the breadboard.
- 4. Connect one end of another jumper wire (Input B) to the input pin of Arduino(e.g., pin3) and other end to the positive rail(+) on the breadboard.
- 5. Enable the power supply to breadboard from arduino by connecting one end of jumper wire to the power pin of Arduino(5V) and other end to the positive rail(+) on the breadboard.

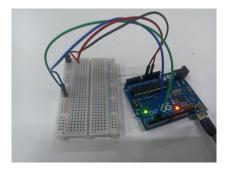


Figure 1: Connections

5 Software

Now write the code which is available in below path and upload to the Arduino.

https://github.com/Pavan2k01/Digital-Design/blob/main/Assembly/Assembly.asm

6 Conclusion

Hence, we have implemented the XOR gate for the given circuit using the code in Assembly language with the help of Arduino.